

# **DIGITAL LOGIC DESIGN LAB (EET1211)**

## **LAB I: Introduction to different ICs and examine the operation of logic gates**

**Siksha 'O' Anusandhan (Deemed to be University), Bhubaneswar**

<b>Branch:</b>	<b>Section:</b>	<b>Subgroup No.:</b>
<b>Name</b>	<b>Registration No.</b>	<b>Signature</b>

**Marks: \_\_\_\_/10**

**Remarks:**

**Teacher's Signature**

## I. Objective:

1. Investigation of the logic behaviour of various gates:

- a) 7400 quadruple two-input NAND gates
- b) 7402 quadruple two-input NOR gates
- c) 7404 hex inverters
- d) 7408 quadruple two-input AND gates
- e) 7432 quadruple two-input OR gates
- f) 7486 quadruple two-input XOR gates

2. Using a single 7400 IC, connect a circuit that produces


- a) An inverter.
- b) A two-input AND.
- c) A two-input OR.
- d) A two-input XOR.

## II. Pre-lab:

1. Logic behaviour of Logic gates


a. Quad two-input NAND gates

A	B	F
0	0	
0	1	
1	0	
1	1	

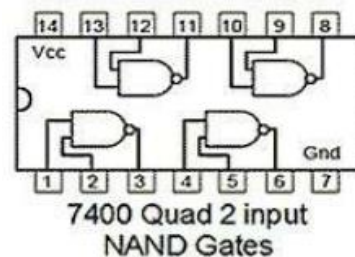


b. Quad two-input NOR gates

A	B	F
0	0	
0	1	
1	0	
1	1	

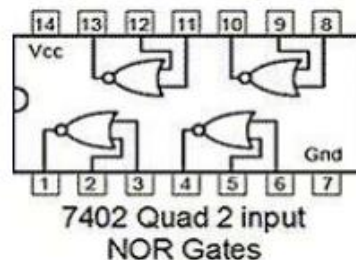


c. Hex inverters

A	F
0	
1	

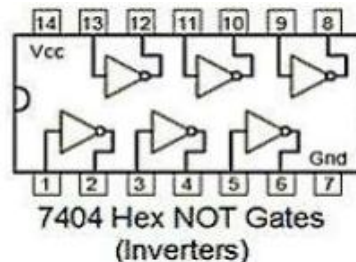


d. Quad two-input AND gates

A	B	F
0	0	
0	1	
1	0	
1	1	

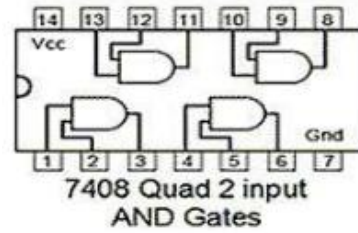


e. Quad two-input OR gates

A	B	F
0	0	
0	1	
1	0	
1	1	

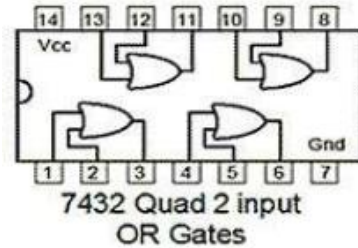

f. Quad two-input XOR gates

A	B	F
0	0	
0	1	
1	0	
1	1	

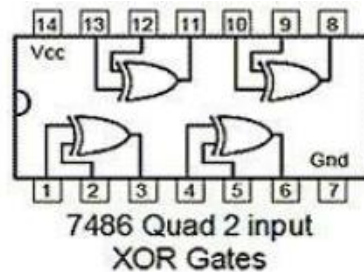

2. Draw the circuit diagram & obtain truth tables for objective 2.

### III. LAB:

#### Components Required:

<u>Sl. No.</u>	<u>Name of the Components</u>	<u>Specification</u>	<u>Quantity</u>

#### Observation:

### IV. CONCLUSION:

### V. POST LAB:

1. What is the voltage range for operation of digital circuits?
2. What is the significance of ground and VCC connection?
3. Which gates are known as universal gates & why.