

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB I: Introduction to different ICs and examine the operation of logic gates

Siksha 'O' Anusandhan (Deemed to be University), Bhubaneswar

Branch: CSE	Section: 2341211	Subgroup No.: 07
Name	Registration No.	Signature
Suryamadhab Moharana	2341013398	Suryamadhab Moharana

Marks: ____/10

Remarks:



Teacher's Signature

I. OBJECTIVE:

1. Investigation of the logic gates ~~of~~ behaviour of various gates.

- a) 7400 quaduple two-input NAND gate.
- b) 7402 quaduple two-input NOR gate.
- c) 7404 hex inverters.
- d) 7408 quaduple two-input ~~AND~~ AND gate.
- e) 7432 quaduple two-input OR gate.
- f) 7486 quaduple two-input XOR gate.


2. Using a single 7400 IC, connect a circuit that produces

- a) An inverter
- b) A two-input AND
- c) A two-input OR
- d) A two-input XOR

11. PRE-LAB :-


1. Logic behaviours of logic gates.

a. Quad two-input NAND gate.

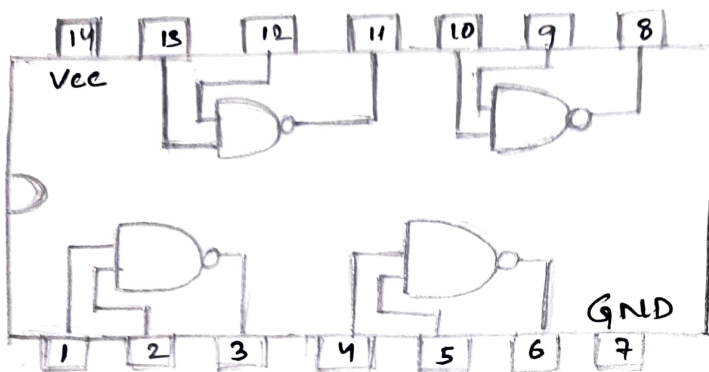


A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

b) Quad two-input NOR gate

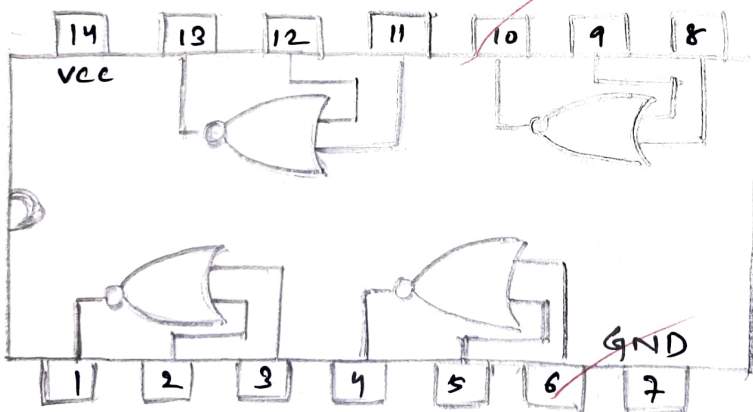


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

c) Hex inverters:-

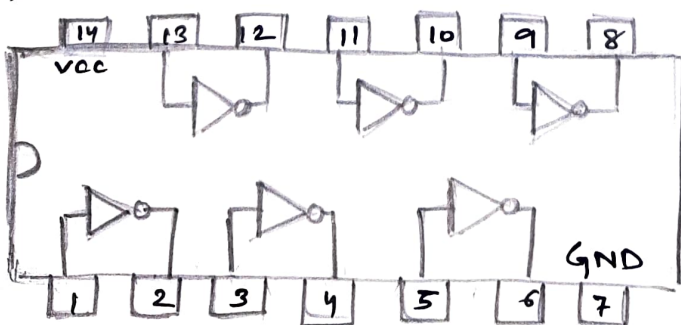


A	F
0	1
1	0

d) Quad two-input AND gate:

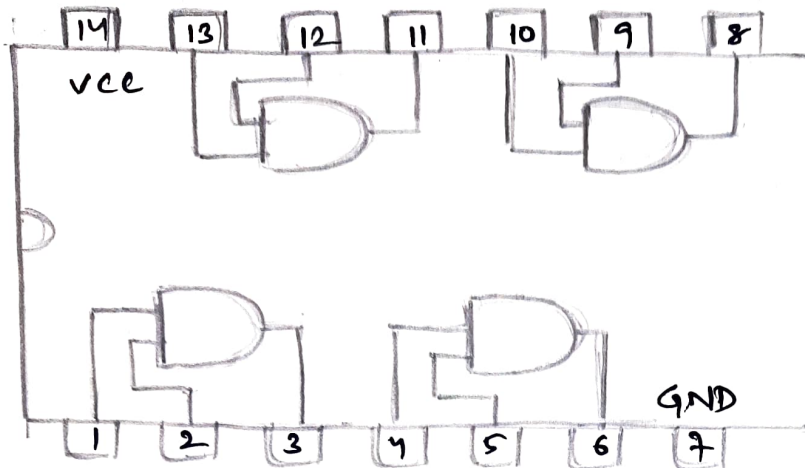


A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

e) Quad two-input OR gate:

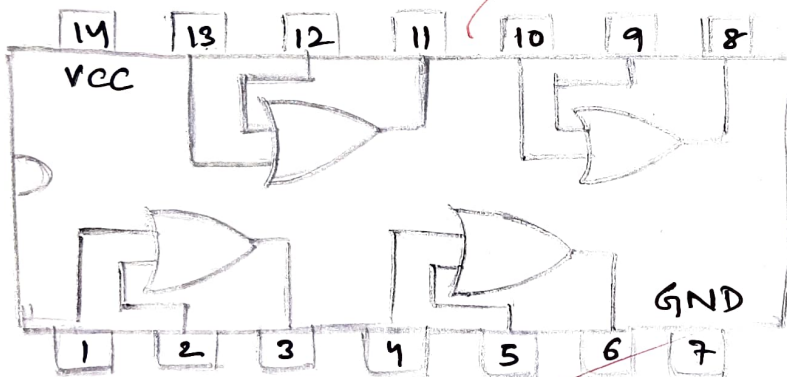

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

f) Quad two-input XOR gate:

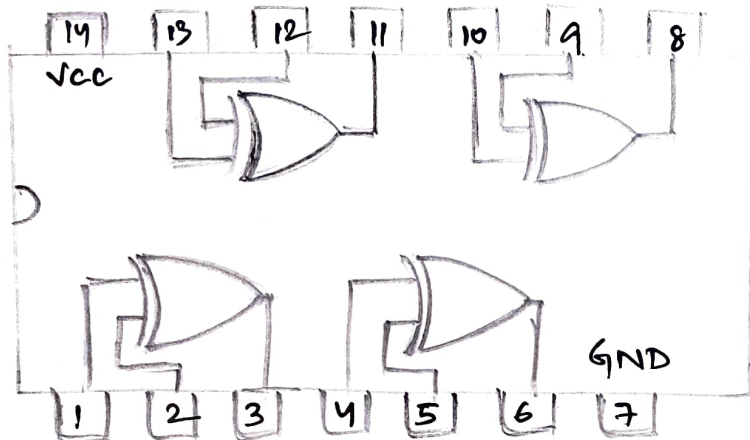


A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

II. PRE-LAB:-


2. Draw the circuit diagram and obtain truth table for objective 2.

a) An inverter using 7400 IC.

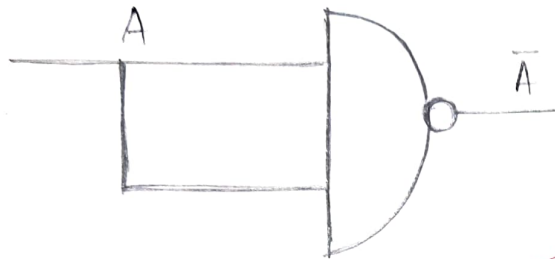


A	F
0	1
1	0

b) A two-input AND using single 7400 IC.

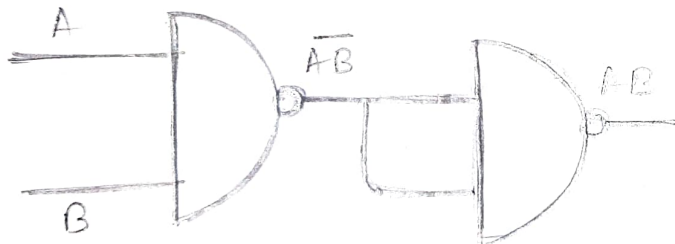


A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

c) A two input OR using single 7400 IC.

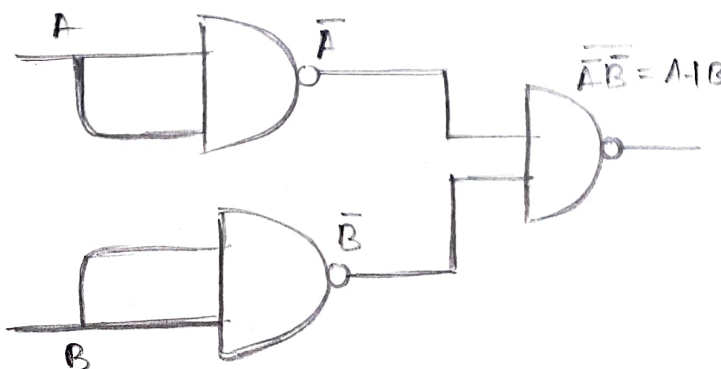

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

d) A two-input XOR using 7400 IC.

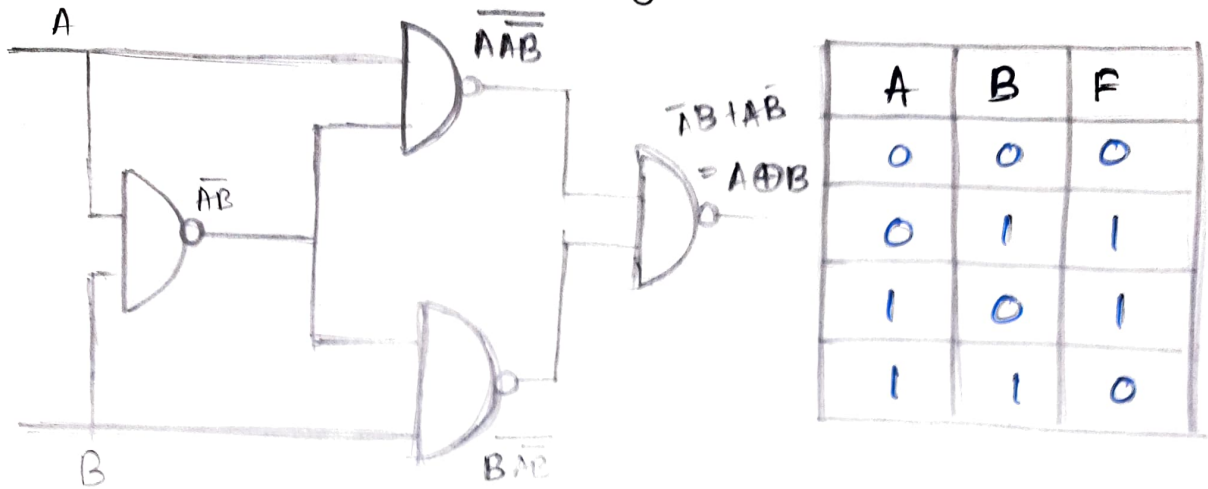

III LAB :-

Components Required :-

Sl.no	Name of the Component	Specification	Qty.
1	Universal Trainer Kit	Microlab II	1
2	Quad two input-NAND gate	IC 7400	1
3	Quad two-input NOR gate	IC 7402	1
4	Quad two-input NOT gate	IC 7404	1
5	Quad two-input AND gate	IC 7408	1
6	Quad two-input OR gate.	IC 7432	1
7	Quad two input XOR gate	IC 7486	1
8	Connecting wire	23SWG	As per requirement


Observation :-

Objective 1 :-

Sl. no.	IC	Pin No.		Status
		I/P	O/P	
1	7400	1, 2	3	Working
2	7402	2, 3	1	Working
3	7404	1	2	Working
4	7408	13, 12	11	Working
5	7432	4, 5	6	Working
6	7486	10, 9	8	Working


Objective - 2 :-

a) An inverter using single 7400 IC.

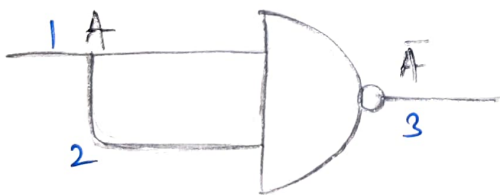


A	F
0	1
1	0

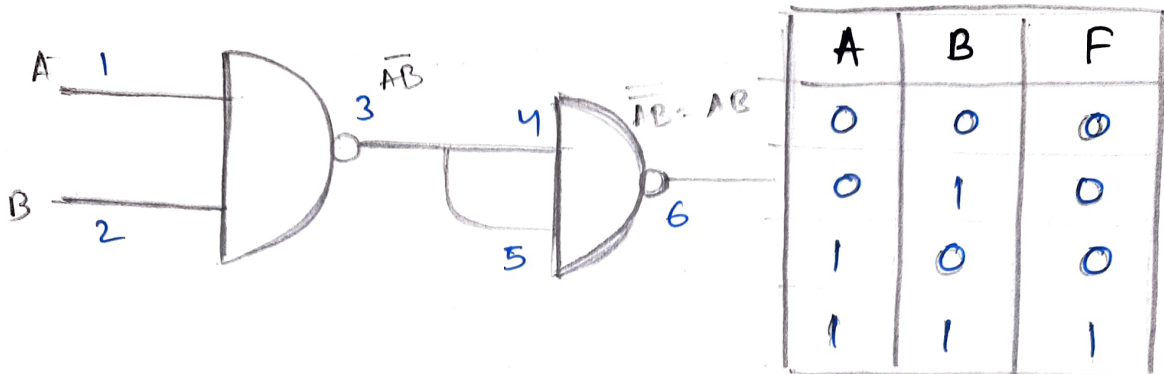
b) A two input AND gate using single 7400 IC.



c) A two input OR using 7400 IC.

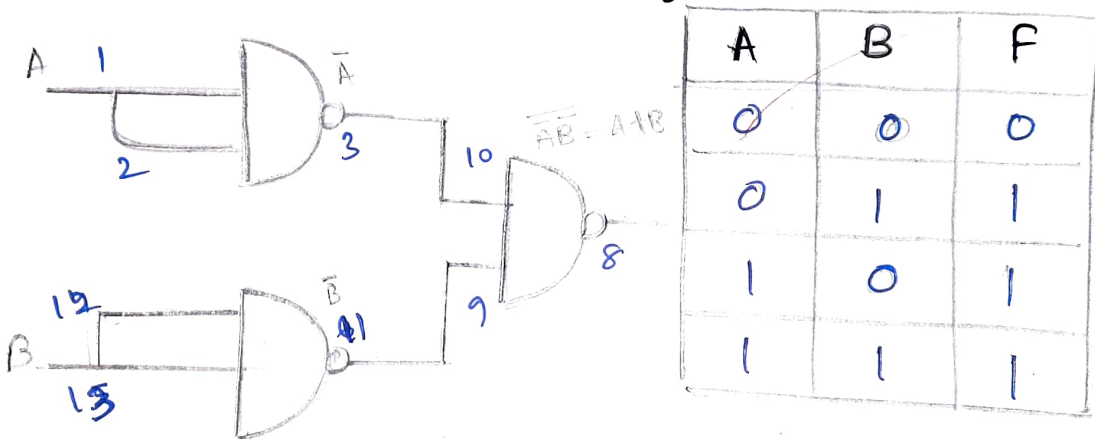

d) A two input XOR using 7400 IC.

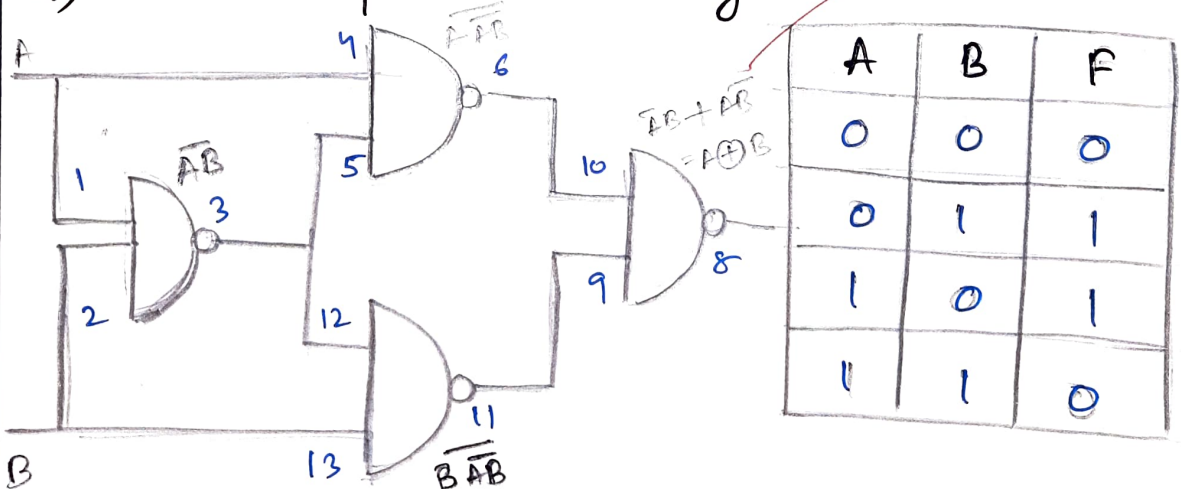

IV CONCLUSION:-

1. In objective 1, we have concluded that all the pins at the provided ICs are working properly and showing the proper output.
2. In objective 2; we have concluded that NAND gate is an universal gate because using it, we can construct AND gate, NOT gate, OR gate, and XOR gate.
3. Also, we have concluded that by analyzing their workings and found out their respective truth table.

V. POST LAB :-

1. What is the voltage range for operation of digital circuits?

Ans. is the voltage range for operation of digital circuits.

2. What is the significance of ground and VCC connection?

Ans. Ground is connected to 0V, connected at pin No. 7, used to establish a

common reference point for all voltage measurement.

V_{cc} is connected to 5V at pin no. 14 which provides voltage to the circuit.

$\therefore V_{cc}$ is higher wrt. ground, it may be +ve or -ve.

3. Which gates are known as universal gates and why?

Ans. NAND gate and NOR gates are called universal gates because by using these, we can form / construct all other gates.